

Notes: Introduction to ARM CortexTM-M Microcontrollers

K

November 1, 2020

Contents

1	Introduction to Computer Electronics	2
1.1	Review of Electronics	2

1 Introduction to Computer Electronics

1.1 Review of Electronics

V = Voltage (Volts), I = Current (Amperes), R = Resistance (Ohms/ Ω)

$$V = IR, I = \frac{V}{R}, R = \frac{V}{I}$$

- Voltage
 - potential to cause current to flow, measured between two places
 - has polarity
- Current
 - has direction
- If the electron flow has stopped resistance is infinite, no electrons flow
- If electrons flow freely, resistance is not zero, but some finite amount
- As resistance varies so does current
- potential is defined as the voltage difference between two places
- current/Flow has direction
 - Low resistance, High current
 - High resistance, Low current
 - Example: Temperature Movement
 - * $\text{Flow} = \frac{T_1 - T_2}{\text{Resistance}}$
 - * T = Temperature
- R-Value
 - used in insulation put in walls and ceiling of a house
 - given in units per square area, e.g. $m^2 \cdot ^\circ C/w$
 - amount of heat flow across a wall:
 - * $\text{Flow} = \frac{\text{Area} \cdot (T_1 - T_2)}{\text{R-Value}}$
 - * T = Temperature
- Power
 - P in watts
 - does not have power or direction

P =Power(watts), V =Voltage(Volts), I =Current(Amperes)

$$P = VI, P = \frac{V^2}{R}, P = I^2 \cdot R$$

- Energy
 - E in joules
 - stored in a battery

- has neither polarity or direction

$$E = \text{Energy(Joules)}, V = \text{Voltage(Voltage)}, I = \text{Current(Amperes)}, t = \text{time(seconds)}$$

$$E = VIt, E = Pt$$

- Switch

- used to modify the behavior of a circuit
- ON
 - * closed, resistance is 0, current flows
 - * resistance of a switch is less than 0.1Ω , assume 0 in most cases
- OFF
 - * open, resistance is ∞ , no current will flow
 - * resistance if greater than $100M\Omega$, close to ∞ therefore assume ∞

- Rules for solving voltages and currents in a circuit compromised with batteries, switches, and resistors

- **Current always flows in a loop**
 - * When there is no loop, no current can flow
- **Kirchoff's Voltage Law (KVL)**
 - * The sum of the voltages around the loop is zero
- **Kirchoff's Current Law (KCL)**
 - * The sum of the currents into a node equal the sum of the currents leaving a node
- **Observation:** If at all possible, draw the circuit so current flows down across the resistors and switches. As a secondary rule have currents go left to right across resistors and switches.
- **Series Resistance**
 - * If resistor $R1$ is in series with resistor $R2$, this combination behaves like one resistor with a value equal to $R1 + R2$
 - * V equals $V1 + V2$
 - * By KCL currents through the two resistors are the same
- **Voltage Divider Rule**
 - *

$$V2 = I \cdot R2$$

$$= (V/R) \cdot R2$$

$$= V * R2 / (R1 + R2)$$

- * The following are equivalent:



